

CE-1901 - Dr. Durant - Quiz 3
Fall 2015, Week 3

1. (2 points) Draw a truth table for function that outputs 1 iff the 3-bit signed input, abc , equals -2, 0, or 1.

ON PRINTER
FIX:
- 8th row
- -1

	$a_2 a_1 a_0$	f
0	000	1
1	001	1
2	010	0
3	011	0
-4	100	0
-3	101	0
-2	110	1
-1	111	1

2. (1 point) Write the canonical sum-of-products (SOP) equation for your truth table.

$$z = \bar{a}_2 \bar{a}_1 \bar{a}_0 + \bar{a}_2 \bar{a}_1 a_0 + a_2 a_1 \bar{a}_0 + a_2 a_1 a_0$$


(-1/2) Or instead of 1/2 selected

3. (1 point) Write the canonical SOP equation in sum-of-minterms (Σ) form.

$$z(a_2, a_1, a_0) = \Sigma(m_0, m_1, m_6, m_7) = m_0 + m_1 + m_6 + m_7 = \Sigma_m(0, 1, 6, 7)$$

any 1 of these is correct

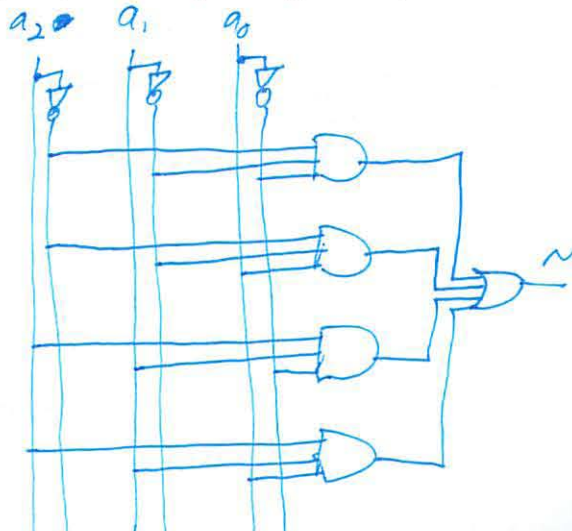4. (1 point) Draw the gate diagram for your canonical SOP equation.



5. (1 point) Write the canonical product-of-sums (POS) equation for your truth table.

$$z = (a_2 + \bar{a}_1 + a_0)(a_2 + \bar{a}_1 + \bar{a}_0)(\bar{a}_2 + a_1 + a_0)(\bar{a}_2 + a_1 + \bar{a}_0)$$


Not's go where 1s are $M_5 = 101$

~~(-1/2)~~ $(-1/2)$ is not a 0s

6. (1 point) Write the canonical POS equation in product-of-maxterms (Π) form.

$$\begin{aligned} z(a_2, a_1, a_0) &= \Pi(M_2, M_3, M_4, M_5) \quad | \text{ correct, only need '1'} \\ &= \Pi_M(2, 3, 4, 5) \\ &= M_2 M_3 M_4 M_5 \quad \leftarrow \text{ yes, but not in } \Pi \text{ form} \end{aligned}$$

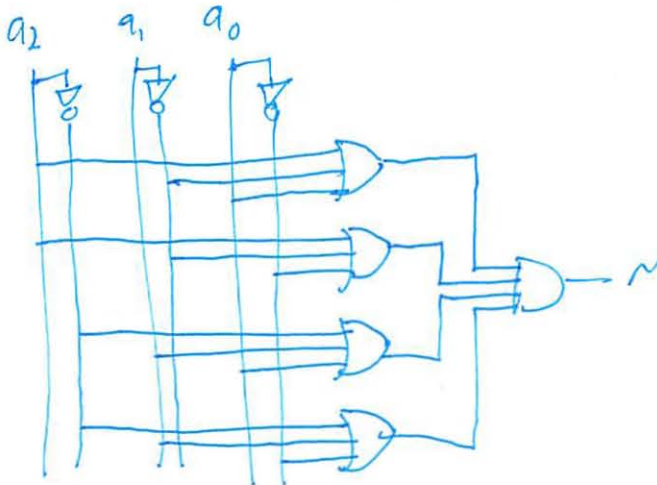7. (1 point) Draw the gate diagram for your canonical POS equation.



8. (2 points) Draw an ideal timing diagram for your function with the input progressing from -4 to +3.

