

Name Answers

CE-1901-11 - Dr. Durant - Quiz 3
Fall 2016, Week 3

1. (1 point) Explain why a digital circuit might not operate properly if $V_{OH} < V_{IH}$.

The voltage of an output of 1 is guaranteed to be at least V_{OH} . Let it exactly equal V_{OH} . When received, the signal is interpreted as 1 if it is at least V_{IH} , which ~~is~~ is $V_{OH} \geq V_{IH}$. But, we are given $V_{OH} < V_{IH}$, which is contradictory. Therefore, we did not receive a value of 1.

2. (2 points) State and explain why either a (relatively) positive or negative charge must present at the gate of an NMOS transistor (specifically, an n-channel enhancement mode MOSFET [metal-oxide-semiconductor field-effect transistor]) in order for current to flow between the drain and the source?

positive charge, attracts negative electrons into the channel, allowing electrical current to flow since this is an n-channel FET

3. (2 points) Complete a truth table for function that outputs 1 iff the 3-bit input, $a_2a_1a_0$ is a palindrome (it reads the same left-to-right as it does right-to-left).

a_2	a_1	a_0	r
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

4. (1 point) Write the **canonical** sum-of-products (SOP) equation for your truth table.


$$z = \bar{a}_2 \bar{a}_1 \bar{a}_0 + \bar{a}_2 a_1 \bar{a}_0 + a_2 \bar{a}_1 a_0 + a_2 a_1 a_0$$

(= $a_2 \odot a_0$, but this is not canonical)


5. (1 point) Write the canonical SOP equation in **sum-of-minterms** (Σ) form.

$$z(a_2, a_1, a_0) = \Sigma_m(0, 1, 5, 7)$$

 6. (1 point) Draw the **gate diagram** for your canonical SOP equation.



 7. (2 points) Draw an **ideal timing diagram** (like Quartus simulation output) for your function with the input progressing through all possible values in a logical order.



Name Answers

CE-1901-12 - Dr. Durant - Quiz 3
Fall 2016, Week 3

1. (1 point) Explain why $V_{OL} < V_{IL}$ is a requirement for the proper operation of a digital circuit.

If this condition is violated then the transmitted voltage representing a 0 can be higher than the maximum acceptable value (V_{IL}) for a receiver to interpret it as a 0, resulting in an incorrect interpretation.

2. (2 points) Explain what it means to say that transistors are active devices (as opposed to passive devices). Recalling the light switch example might be helpful.

They control or "switch" energy that can be greater than the input energy used for control. (Thus they require a separate power source from the controlling input.)

3. (2 points) Complete a truth table for function that outputs 1 iff the 3-bit unsigned number, $a_2a_1a_0$, is less than 4.

a_2	a_1	a_0	r
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

4. (1 point) Write the **canonical** sum-of-products (**SOP**) equation for your truth table.


$$z = \bar{a}_2 \bar{a}_1 \bar{a}_0 + \bar{a}_2 \bar{a}_1 a_0 + \bar{a}_2 a_1 \bar{a}_0 + \bar{a}_2 a_1 a_0$$

($= \bar{a}_2$, but that's not canonical)

5. (1 point) Write the canonical SOP equation in **sum-of-minterms** (Σ) form.

$$z(a_2, a_1, a_0) = \Sigma_m(0, 1, 2, 3)$$

 6. (1 point) Draw the **gate diagram** for your canonical SOP equation.



7. (2 points) Draw an **ideal timing diagram** (like Quartus simulation output) for your function with the input progressing through all possible values in a logical order.

