

CE-1901 - Dr. Durant - Quiz 4
Fall 2015, Week 4


1. (0.5 point) Which of the standard forms is $F = ac' + ab'$ in? POS or SOP

2. (1 point) Apply Boolean algebra, specifically the distributive property, to write the equation in the other standard form

Answer: $F = a(\bar{c} + b)$

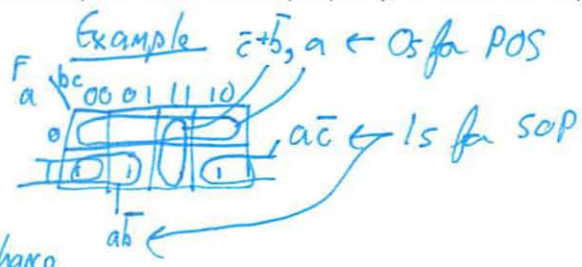Example: DUAL

note this $\rightarrow \bar{F} = \bar{a} + (cb)$
literals inverted since 1s/0s interchange roles



3. (0.5 point) Is the equation in problem 1 in canonical form? Yes or No


not all 3 literals appear in each product term

4. (1 point) Prove that $x' + y' = (xy)'$ using perfect induction. Hint: evaluate both expressions in a truth table and confirm that they agree in all rows.

x	y	\bar{x}	\bar{y}	$\bar{x} + \bar{y}$	xy	$(xy)'$
0	0	1	1	1	0	1
0	1	1	0	1	0	1
1	0	0	1	1	0	1
1	1	0	0	0	1	0


\leftarrow equal

Space for work on problem 10

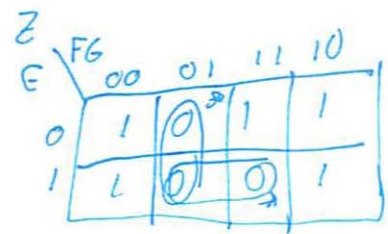

$Z = (F + \bar{G})(\bar{E} + \bar{G})$

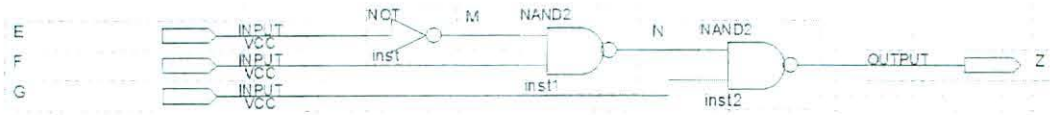5. (2 points) Draw the truth table for the following schematic. Include columns for each intermediate term (all gate outputs); there are more columns than you need in the given table.



E	F	G	M	N	Z
0	0	0	1	1	1
0	0	1	1	1	0
0	1	0	1	0	1
0	1	1	1	0	1
1	0	0	0	1	1
1	0	1	0	1	0
1	1	0	0	1	1
1	1	1	0	1	0

6. (1 point) Write the equation directly from the schematic above

$$Z = \overline{G \bar{E} F}$$

7. (1 point) Write the canonical sum-of-products (SOP) equation based on your truth table above. Don't use a shorthand form.

$$Z = \bar{E}\bar{F}\bar{G} + \bar{E}\bar{F}G + \bar{E}F\bar{G} + E\bar{F}\bar{G} + EF\bar{G}$$

(-1/2) MIN, NOT CAN., SOP

8. (1 point) Write the canonical product-of-sums (POS) equation based on your truth table above. Don't use a shorthand form.

$$Z = (E + F + \bar{G})(\bar{E} + F + \bar{G})(\bar{E} + \bar{F} + \bar{G})$$

(-1/2) NOT I/O INPUT REVERSAL

9. (1 point) Restate the equation above in both Σ and Π notations. Hint: These are based on minterm and maxterm numbers.

$$Z(EFG) = \Sigma_m(0, 2, 3, 4, 6) \quad \text{OR} \quad Z(EFG) = \Sigma(M_0, M_2, M_3, M_4, M_6)$$

$$= \Pi_M(1, 5, 7) \quad \text{OR} \quad \Pi(M_1, M_5, M_7)$$

(-1/4) NO EFG

10. (1 point) On the other side of this sheet, draw a K-map for Z and use the map to determine the simplest (most reduced) equation in product-of-sums form. Reminders: adjacent terms in a K-map may differ in the value of only 1 bit. Start with M_0 in the upper left corner, putting M_1 to the right and M_4 below it. Form largest groups possible. It is okay to cover zeros (terms that are off) more than once in order to form larger groups.