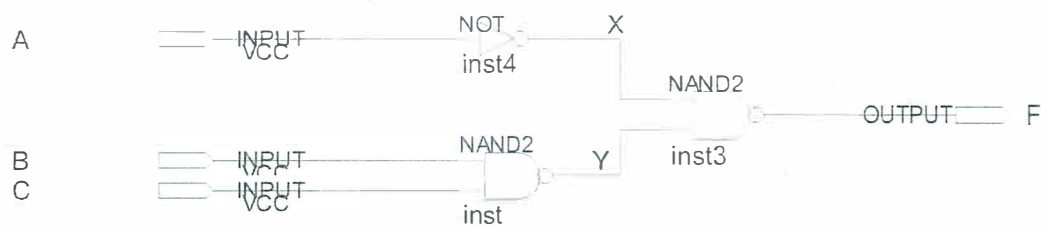


**CE-1901-11 – Dr. Durant – Quiz 4  
Winter 2016-'17, Week 5**

Note: These quiz problems are in 3 groups: problems 1-3, 4, and 5-8.

1. (2 points) **Complete** the truth table for the following schematic. **Include** columns for each intermediate term (all gate outputs).



A	B	C	X	Y	F
0	0	0	1	1	0
0	0	1	1	1	0
0	1	0	1	1	0
0	1	1	1	0	1
1	0	0	0	1	1
1	0	1	0	1	1
1	1	0	0	1	1
1	1	1	0	0	1

2. (1 point) **Write** the equation **directly** from the **schematic** above.

$$F = \overline{\overline{A} \overline{B} C} = \overline{\overline{A}} + \overline{\overline{B} C} = A + BC$$

3. (1 point) **Write** the simpler of the 2 canonical equations (SOP or POS) based on your truth table.

3 Os  $\therefore$  POS is simpler


$$F(ABC) = \prod(M_0, M_1, M_2) = M_0 M_1 M_2 = (A+B+C)(A+B+\overline{C})(A+\overline{B}+C)$$

4. (1 point) **Prove** that  $(AB)' = A' + B'$  using perfect induction. That is, evaluate both expressions in a truth table and confirm that they agree in all rows. Be sure to include all intermediate terms as columns, including NOTs.

AB	A·B	$\overline{A \cdot B}$	$\overline{A}$	$\overline{B}$	A+B
00	0	1	1	1	1
01	0	1	1	0	1
10	0	1	0	1	1
11	1	0	0	0	0

equal

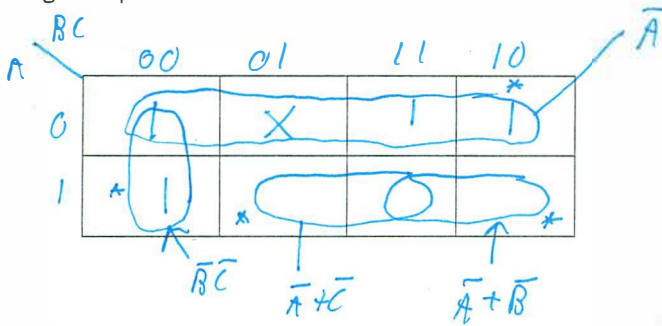5. (2 points) Let  $F(ABC) = \Sigma_m(0, 2, 3, 4) + d(1)$  ( $d$  indicates don't care conditions). Derive the simplest SOP or POS expression for  $F$  using a K-map. **Reminders:** adjacent terms in a K-map may differ in the value of only 1 bit. Start with  $m_0$  in the upper left corner, putting  $m_1$  to the right and  $m_4$  below it. Form largest groups possible. It is okay to cover terms more than once as you form larger implicants.




simplest (due to group of 4)


$$F = \bar{A} + \bar{B}\bar{C} = (\bar{A} + \bar{C})(\bar{A} + \bar{B})$$

in Boolean algebra, + distributes over • (!)

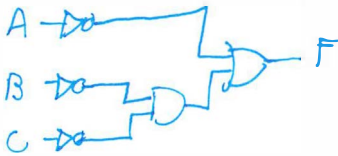6. (1 point) Draw your reduced circuit for  $F$  directly using NOT, AND, and OR gates.



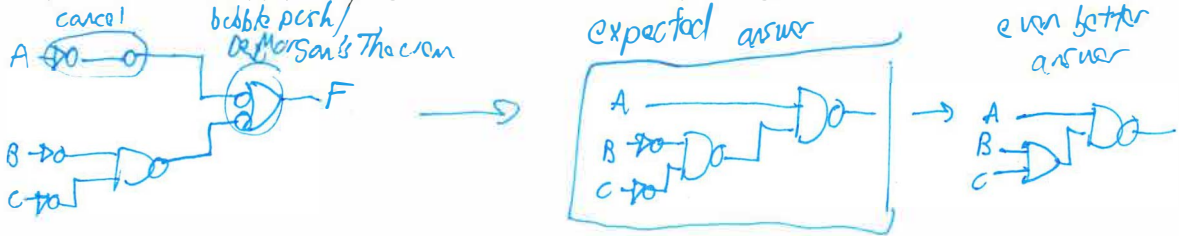7. (1 point) Re-draw it using just (NAND [for SOP] or NOR [for POS]) and NOT gates based on the most simplified form. **Reminders:** The first step is to put 2 NOT gates on every input to the final output. After that, apply DeMorgan's Theorems (bubble pushing).



8. (1 point) **Calculate** the number of transistors needed for **each** of the two reduced equations above.

⑥	3 NOT	6
	1 AND2	6
	1 OR2	6
		<u>18</u>

⑦	Expected	
	2 NOT	4
	2 NAND2	<u>8</u>


*circuits*

Better	
1 OR2	6
1 NAND2	<u>8</u>
	<u>10</u>

**CE-1901-12 – Dr. Durant – Quiz 4**  
**Winter 2016-'17, Week 5**

Note: These quiz problems are in 3 groups: problems 1-3, 4, and 5-8.

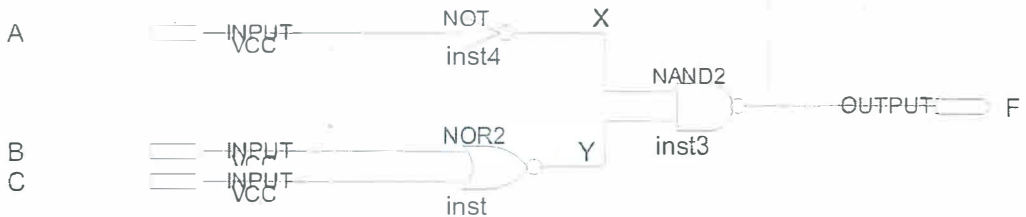1. (2 points) **Complete** the truth table for the following schematic. **Include** columns for each intermediate term (all gate outputs).



A	B	C	X	Y	F
0	0	0	1	1	0
0	0	1	1	0	1
0	1	0	1	0	1
0	1	1	1	0	1
1	0	0	0	1	1
1	0	1	0	0	1
1	1	0	0	0	1
1	1	1	0	0	1

2. (1 point) **Write** the equation **directly** from the **schematic** above.

$$F = \overline{\overline{A} \overline{B} + C} = \overline{\overline{A}} + \overline{\overline{B} + C} = A + (B + C) = A + B + C$$

3. (1 point) **Write** the simpler of the 2 canonical equations (SOP or POS) based on your truth table.

only 1 0, use POS


$$F = A + B + C \quad (\text{1 sum term, canonical})$$

4. (1 point) **Prove** that  $(A+B)' = A'B'$  using perfect induction. That is, evaluate both expressions in a truth table and confirm that they agree in all rows. Be sure to include all intermediate terms as columns, including NOTs.

A	B	A+B	$\overline{A+B}$	$\overline{A}$	$\overline{B}$	$\overline{A} \overline{B}$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

equal

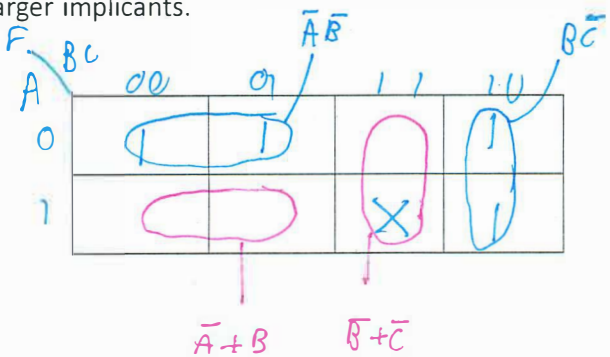5. (2 points) Let  $F(ABC) = \Sigma_m(0, 1, 2, 6) + d(7)$  (d indicates don't care conditions). Derive the simplest SOP or POS expression for F using a K-map. **Reminders:** adjacent terms in a K-map may differ in the value of only 1 bit. Start with  $m_0$  in the upper left corner, putting  $m_1$  to the right and  $m_4$  below it. Form largest groups possible. It is okay to cover terms more than once as you form larger implicants.





$$F = \bar{A}\bar{B} + B\bar{C}$$

$$= (\bar{A}+B)(\bar{B}+\bar{C})$$


*equally complex either is correct*

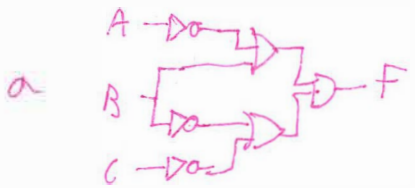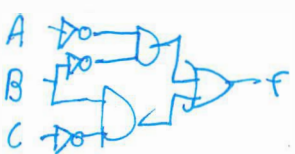6. (1 point) Draw your reduced circuit for F directly using NOT, AND, and OR gates.



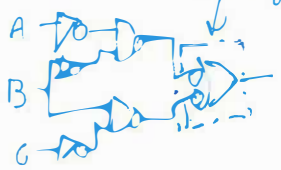7. (1 point) Re-draw it using just (NAND [for SOP] or NOR [for POS]) and NOT gates based on the most simplified form. **Reminders:** The first step is to put 2 NOT gates on every input to the final output. After that, apply DeMorgan's Theorems (bubble pushing).

*following SOP... bubble push / DeMorgan's Theorem*



8. (1 point) **Calculate** the number of transistors needed for **each** of the two reduced circuits above.

5	SOP		7	
3	NOT	6	3	NOT
2	AND2	12	3	NAND2
1	OR2	6		
		<u>24</u>		
				<u>18</u>