
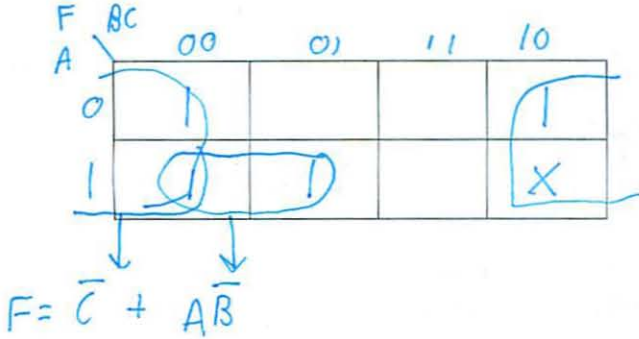


CE-1901 - Dr. Durant - Quiz 5  
Fall 2015, Week 5 Quiz

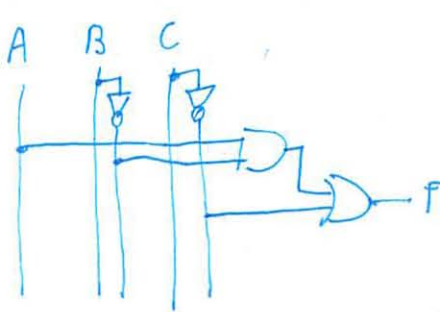1. (2 points) Let  $F(ABC) = \sum_m(0,2,4,5) + d(6)$  (that is,  $m_6$  is a don't care). Derive the simplest SOP expression for  $F$  using a K-map.





2. (1 point) Draw your reduced circuit for  $F$  directly using NOT-AND-OR gates.



(-1/4) *unnecessary A gate*

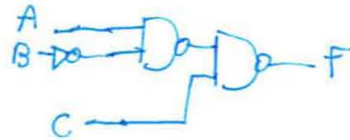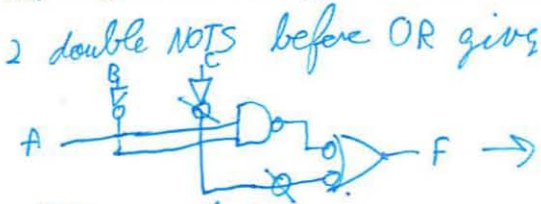3. (2 points) Re-draw it using just NAND and NOT gates in the most simplified SOP form.



(-1) *wrong gate types*  
(-1/2) *AB not reversed*

4. (1 point) Calculate the number of transistors needed for each reduced implementation above.

NOT-AND-OR  
 $2 \times 2 + 6 + 6$   
 $=$   
 16

NAND-NOT  
 $2 \times 4 + 2$   
 $=$   
 10

$$F(WXYZ) = F = (W + \bar{Y})(\bar{X} + \bar{Y})$$

5. (2 points) Draw the K-map that results in  $F(wxyz) = (W+X+Y')(X+Y'+Z)(X'+Y+Z')(W'+X+Z)$ .

	yz	00	01	11	10
wk	00			0	0
	01		0		
	11	0	0	0	0
	10	0			0

		$w + \bar{y}$	$\bar{x} + \bar{y}$		
F	xy	00	01	11	10
w	0		0	0	
	1			0	

(+3/4) exactly 1 of 2 kmap right / 2/5  
 (-1/4) slow groups, o.w. correct

6. (2 points) Draw another map for F and fill in the same 0s as you found above. **Modify** your map so that  $m_5$  is a don't care. **Derive** the simplified POS expression taking advantage of this change.

$m_5$

			0	0
		0	X	
	0	0	X	0
	0			0

	xy	00	01	11	10
w	0		0	0	
	1		0	0	

(-1/2) correct map, but uncorrect group, small error

$$F = \bar{y}$$

7. (1 point) Draw the circuit for the reduced equation that takes advantage of the don't care.

8. (0 points, just for entertainment) **How many** different 3-variable K-maps are possible if no don't cares are used? (That is, how many different ways is it possible to fill the cells of a 3-variable K-map using only 0s and 1s?) How does the answer **change** if don't cares are also used?

3 variables  $\rightarrow 2^3 = 8$  rows in truth table.  
 each of 8 rows can have 1 of 2 values, so  $2^8 = 256$  possible k-maps

with don't cares  
 each of 8 rows can have 1 of 3 (0, 1, x) values, so  $3^8 = 9^4 = 81^2 = 6561$  k-maps