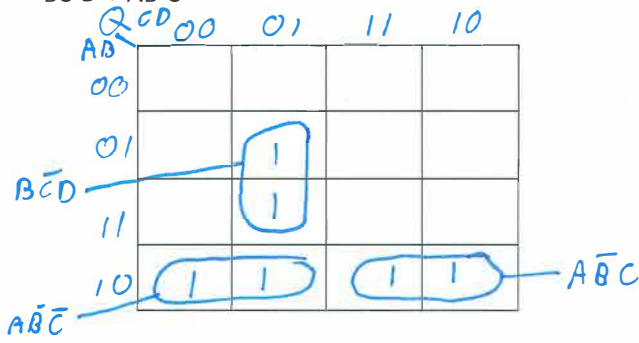


CE-1901-11 - Dr. Durant - Quiz 5
 Winter 2016-'17, Week 6 Quiz

1. (1 point) **Draw** the K-map (including implicants) that goes with the following equation: $Q = AB'C + BC'D + AB'C'$



2. (1 point) **Explain** whether the K-map above was used to generate the simplest possible SOP equation (assume there were no don't cares).


not simplest. Bottom row should be $A\bar{B}$. C cancels.

3. (3 points) MUXes


- a. (1 point) **Write** the logic equation for the 4:1 MUX, $y = f(s_{1..0}, d_{0..3})$. Remember that there is a product term for each of the data terms; this product term checks all values of s to make sure they match the term's corresponding s -minterm.

$$y = \bar{s}_1 \bar{s}_0 d_0 + \bar{s}_1 s_0 d_1 + s_1 \bar{s}_0 d_2 + s_1 s_0 d_3$$

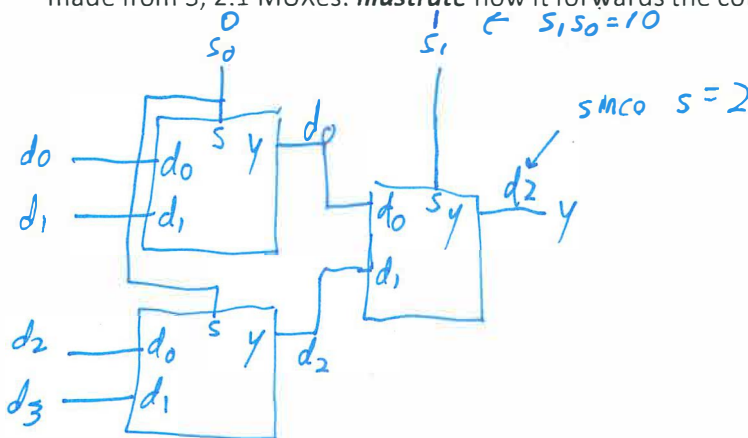- b. (2 points) Using a block diagram (without the internal gates) **show** how a 4:1 MUX can be made from 3, 2:1 MUXes. **Illustrate** how it forwards the correct d input when $s = 2 = 10_2$.



 
4. (4 points) Simplification and implementation: $F(abcd) = \Sigma_m(1, 5, 6, 7, 9, 13, 11, 15) + d(8, 10)$
 a. (2 points) **Draw** the K-map and use it to **derive** a simplified SOP expression taking advantage of these don't cares.



$$F = \bar{C}D + \bar{A}BC + AD$$

The 4th term is redundant.
 The X don't help here.

 - b. (1 point) **Draw** the NOT-NAND-NAND form of the SOP circuit. Hint: Begin by placing 2 NOTs in series on each input to the OR.



- c. (1 point) **Why** is the NOT-NAND-NAND form usually preferable to the NOT-AND-OR form?

requires fewer transistors


5. (1 point) **Contrast** the information you need to write a with-select statement with that needed for a direct assignment (e.g., $f \leftarrow (a \text{ and not } b) \text{ or } c$);

with-select: just need truth table

direct assignment: need equation

CE-1901-12 - Dr. Durant - Quiz 5
Winter 2016-'17, Week 6 Quiz

 1. (1 point) **Draw** the K-map (including implicants) that goes with the following equation: $Q = A'C' + BCD' + A'C$.



2. (1 point) **Explain** whether the K-map above was used to generate the simplest possible SOP equation (assume there were no don't cares).


no, $A'C + A'C = \bar{A}$ (PI of 8)
 \uparrow
 prime implicant

3. (3 points) MUXes

- a. (1 point) **Write** the logic equation for the 4:1 MUX, $y = f(s_{1..0}, d_{0..3})$. Remember that there is product term for each of the data terms; this product term checks all values of s to make sure they match the term's corresponding s -minterm.


$$y = \bar{s}_1 \bar{s}_0 d_0 + \bar{s}_1 s_0 d_1 + s_1 \bar{s}_0 d_2 + s_1 s_0 d_3$$

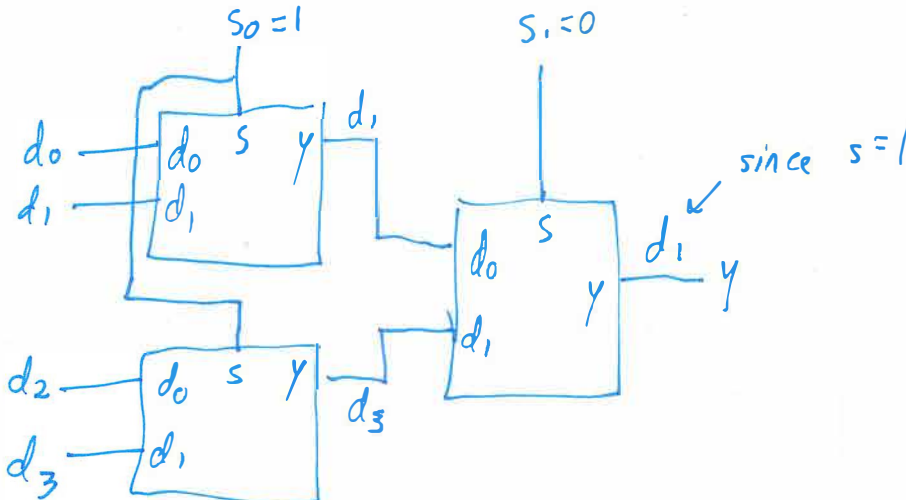- b. (2 points) Using a block diagram (without the internal gates) **show** how a 4:1 MUX can be made from 3, 2:1 MUXes. **Illustrate** how it forwards the correct d input when $s = 1 = 01_2$.



4. (4 points) Simplification and implementation: $F(abcd) = \sum_m(1, 5, 6, 7, 9, 13, 11, 15) + d(12, 14)$

 a. (2 points) **Draw** the K-map and use it to **derive** a simplified SOP expression taking advantage of these don't cares.




The 3 essential PIs cover all the 1s!

$$F = \bar{c}d + bc + ad \leftarrow$$

$$= (\bar{c} + a)d + bc$$

 b. (1 point) **Draw** the NOT-NAND-NAND form of the SOP circuit. Hint: Begin by placing 2 NOTs in series on each input to the OR.



c. (1 point) **Why** is the NOT-NAND-NAND form usually preferable to the NOT-AND-OR form?

NANDs have 2 fewer transistors than AND/OR for a given number of inputs.

5. (1 point) **Contrast** the purpose of the entity section with the architecture section of a VHDL file.

entity: specify just what the inputs & outputs are

architecture: explain how to implement a circuit, eg. truth table or which gates to use & how to connect them