 


CE-1901 - Dr. Durant - Quiz 6
Fall 2015, Week 6 Quiz

1. (6 points) Simplification and implementation: $F(abcd) = \sum_m(1, 3, 4, 5, 6, 7, 9, 11, 12) + d(13, 14)$



all 1s covered w/ essential PIs

$$F = \bar{a}d + \bar{b}d + b\bar{d}$$

c not needed!

here I omitted $\bar{a}b$ for simplicity, but, including it instead of $\bar{a}d$ is equally valid

- b. (1 point) **Draw** the SOP schematic using NOT-AND-OR gates.




* aka if all vars have NOT, any use w/o NOT since contamination delay of 2

- c. (0.5 point) **What** path of gates is involved in the contamination delay (shortest path) of this circuit? (illustrate in part b)
 d. (0.5 point) **What** path of gates is involved in the propagation delay (critical path) of this circuit? (illustrate in part b)
 e. (0.5 point) **How** many CMOS transistors does this require? Show your calculations.

$$\begin{array}{l} 2 \text{ NOT @ } 2 \\ 3 \text{ AND } 2 @ 6 \\ 1 \text{ OR } 3 @ 8 \end{array} \left. \begin{array}{l} 6 \\ 18 \\ 8 \end{array} \right) \begin{array}{l} 6 \\ 30 \\ 32 \end{array}$$

 - f. (1 point) **Draw** the NOT-NAND-NAND form of the SOP circuit. Hint: Begin by placing 2 NOTs in series on each input to the OR.



- g. (0.5 point) **How** many CMOS transistors does this require? Show your calculations.

$$\begin{array}{l} 3 \text{ NOT @ } 2 = 6 \\ 3 \text{ NAND } 2 @ 4 = 12 \\ 1 \text{ NAND } 3 @ 6 = 6 \end{array} \left. \begin{array}{l} 6 \\ 12 \\ 6 \end{array} \right) \begin{array}{l} 6 \\ 24 \\ 24 \end{array}$$

- h. (0 points, extra challenge) Factor your result from (a) and apply bubble pushing to show how you can make an even smaller implementation of F than what you found above.

$$F = d(\bar{a} + \bar{b}) + b\bar{d} = d\bar{a}\bar{b} + b\bar{d} = \overline{\overline{d\bar{a}\bar{b}}} + \bar{b}\bar{d} = \overline{\overline{d\bar{a}\bar{b}}} \bar{b}\bar{d}$$

$$\begin{array}{l} 1 \text{ NOT @ } 2 = 2 \\ 4 \text{ NAND } 2 @ 4 = 16 \\ \hline 18 \end{array}$$


there is also $b \oplus d$, but XOR is a large gate in CMOS.

2. (2 points) MUXes

- a. (2 points) **Write** the logic equation for the 4:1 MUX, $y = f(s_{1..0}, d_{0..3})$. Remember that there is a product term for each of the data terms; this product term checks all values of s to make sure they match the term's corresponding s -minterm.

$$y = \bar{s}_1 \bar{s}_0 d_0 + \bar{s}_1 s_0 d_1 + s_1 \bar{s}_0 d_2 + s_1 s_0 d_3$$

 - b. (2 points) Using a block diagram **show** how a 4:1 MUX can be made from 3, 2:1 MUXes.



(-1/4) s_1, s_0 reversed
 (-1/2) internal signals mostly unlabeled

3. (2 points) Signed Numbers

- a. **Calculate** the range of a 12-bit **signed** number. Remember, half of the numbers are negative.

$2^{11} = 2048$ negative numbers, 1 zero, 2047 positives

$$[-2048, 2047]$$

don't negate, 2's comp. represents + & - numbers

- b. **Convert** +5 and -4 into their 4-bit 2's complement representations and confirm that their sum is +1.

5 0101
 flip 1010
 +1 1011


4 0100
 flip 1011
 +1 1100 $\rightarrow -4$

$$\begin{array}{r} 0101 \quad 5 \\ + 1100 \quad -4 \\ \hline 0001 \quad 1 \end{array}$$

CE-1901 - Dr. Durant - Quiz 6
Fall 2015, Week 6 Quiz


ALTERNATE
PROBLEM →
NOT GIVEN
ON QUIZ

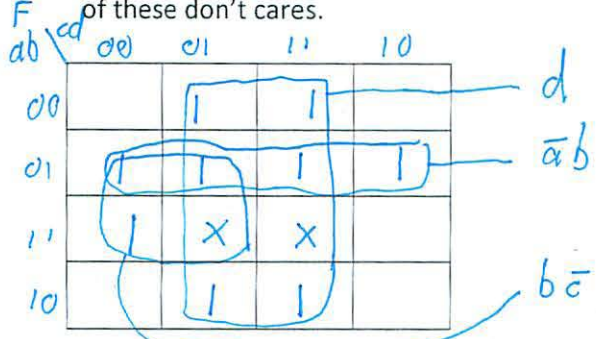(6 points) Simplification and implementation: $F(abcd) = \Sigma_m(1, 3, 4, 5, 6, 7, 9, 11, 12) + d(13, 14) + d(15)$



$F = \bar{a}b + b\bar{c} + d$

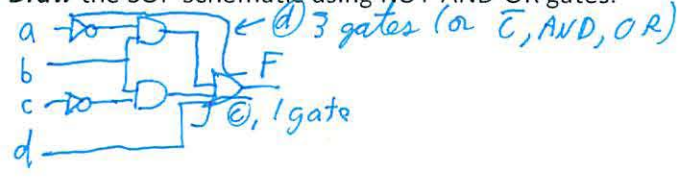
b. (1 point) Draw the SOP schematic using NOT-AND-OR gates.



- c. (0.5 point) What path of gates is involved in the contamination delay (shortest path) of this circuit? (illustrate in part b)
- d. (0.5 point) What path of gates is involved in the propagation delay (critical path) of this circuit? (illustrate in part b)
- e. (0.5 point) How many CMOS transistors does this require? Show your calculations.

$2 \times 2 = 4$ for NOT
 $2 \times 6 = 12$ for AND2
 $1 \times 8 = 8$ for OR3

 f. (1 point) Draw the NOT-NAND-NAND form of the SOP circuit. Hint: Begin by placing 2 NOTs in series on each input to the OR.




g. (0.5 point) How many CMOS transistors does this require? Show your calculations.

$6 = 3 \times 2$ for NOT
 $8 = 2 \times 4$ for NAND2
 $6 = 1 \times 6$ for NAND3

20

 h. (0 points, extra challenge) Factor your result from (a) and apply bubble pushing to show how you can make an even smaller implementation of F than what you found in (e).

$F = b(\bar{a} + \bar{c}) + d = b\bar{a}\bar{c} + d = \overline{\overline{b\bar{a}\bar{c}d}}$



$3 \times \text{NAND2} \rightarrow 12$
 $2 \times \text{NOT} \rightarrow 2$
 Total: 14

above