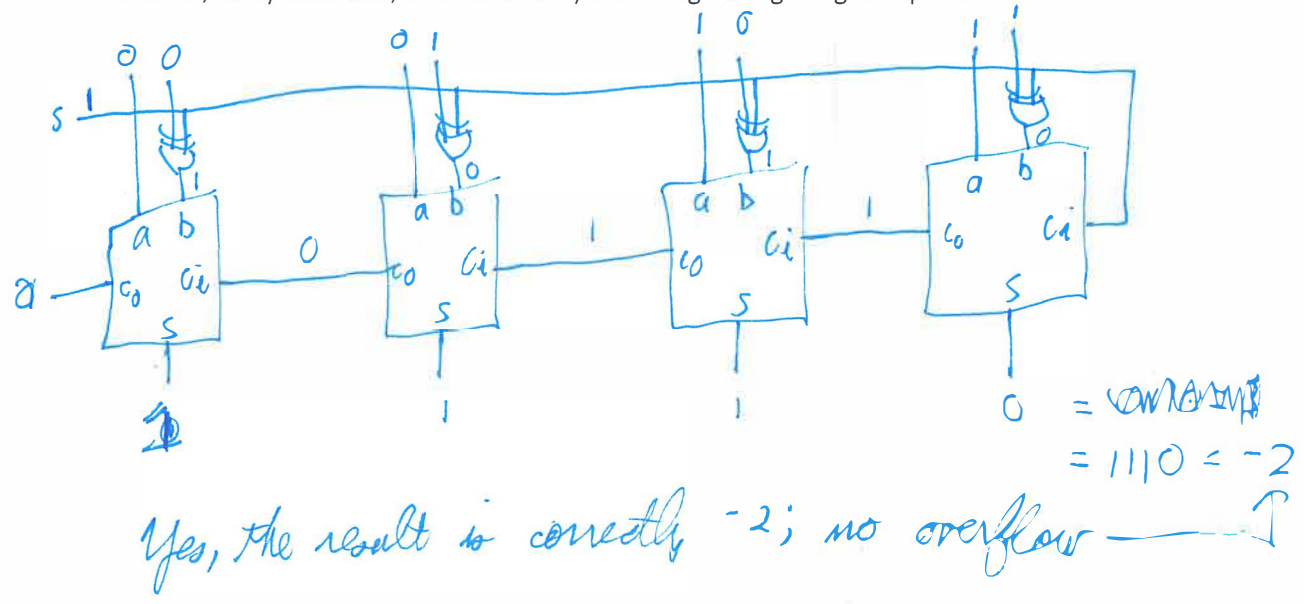


CE-1901-11 - Dr. Durant - Quiz 7
 Winter 2016-'17, Week 8 Quiz

1. (6 points) Subtraction
 - a. (4 points) **Draw** the block diagram for the 4-bit ripple-carry adder-subtractor (RCAS4). **Use** full adder (FA) blocks. **Hint:** You need a "s"ubtract input and 4 XOR2 gates.
 - b. (2 points) **Label** the inputs to your RCAS4 so that it is subtracting B=5 from A=3. **Show the logic value** of every node in the circuit (but not the internal details of the FAs). Comment on whether your answer is correct ($3 - 5 = -2$).
2. (4 points) ALUs
 - a. (2 points) Using 4-bit unsigned numbers, **calculate** the XNOR of the decimal numbers 10 and 6. **Show** your work.
 - b. (2 points) **Explain** the purpose of the LE (logic extender) in calculating a logical function in the ALU designed in class. Be sure to **include** what the other key components (arithmetic extender, carry extender, and full adder) are doing during a logical operation.



② ④ A 10 1010
 B 06 00110
 3 ← 0011

⑥ When a logical operation is selected, the LE, with inputs $a \oplus b$, calculates the result. The other extenders all output 0 so that the RCA adds 0 to the result, leaving it correct & unmodified

CE-1901-12 - Dr. Durant - Quiz 7
Winter 2016-'17, Week 8 Quiz


1. (6 points) Subtraction

- a. (4 points) **Draw** the block diagram for the 4-bit ripple-carry adder-subtractor (RCAS4). Use full adder (FA) blocks. **Hint:** You need a "s" subtract input and 4 XOR2 gates.
- b. (2 points) **Label** the inputs to your RCAS4 so that it is subtracting $B = -3$ from $A = 6$. **Show the logic value** of every node in the circuit (but not the internal details of the FAs). **Assume** that you're using the same system for interpreting the output as for the inputs. Comment on whether your answer is correct ($6 - -3 = 9$?).

$-3 = 1101$

2. (4 points) ALUs

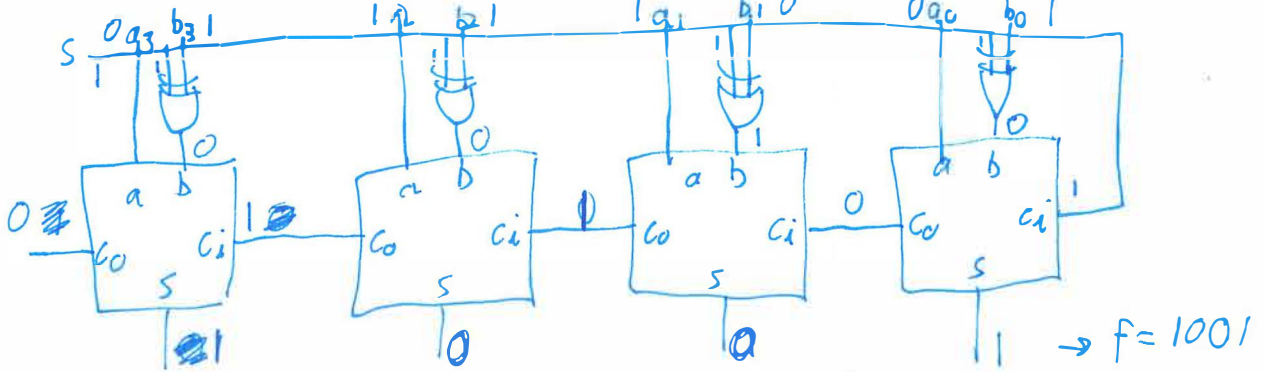- a. (2 points) Using 4-bit unsigned numbers, **calculate** the XOR of the decimal numbers 5 and 12. **Show** your work.
- b. (2 points) **Explain** the purpose of the CE (carry extender) in the ALU designed in class. Be sure to **include** at least one example each of when the CE must output 0 and 1.



Signed system, so $1001 = -7 \rightarrow$ signed overflow.
Error = $-7 - 9 = -16 = -(2^4)$

②

$$\begin{array}{r} 5 \quad 0101 \\ +12 \quad 01100 \\ \hline 9 \leftarrow 1001 \end{array}$$

③ Generate c_0 for the specified operation, eg. 0 for $A+B$ but 1 for $A-B$ for 2's complement operation on B.