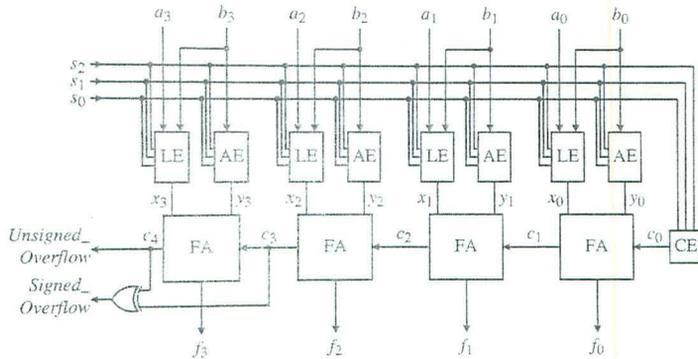


CE-1901-11 - Dr. Durant - Quiz 8
Fall 2016, Week 9 Quiz

1. (6 points) ALUs



a. (2 points) **Complete** the following table for a 4-operation ALU (an 8-operation ALU is shown for reference):

S	Operation	Expression	LE (FA:a)	AE (FA:b)	CE (FA0:c _i)
0	Decrement	--A	A	0 1	0 1
1	XOR	$A \oplus B$	$A \oplus B$	0	0
2	Subtract	$A - B$	A	\bar{B}	1
3	Add	$A + B$	A	B	0

b. (2 points) **Explain** why the given extender values for decrement are correct. **Provide** an example where the input $A = 1010$.

c. (2 points) **Design** the LE using a K-map.

(b)
$$\begin{array}{r} 11100 \leftarrow CE \rightarrow c_0 \\ 1010 \leftarrow LE \rightarrow \text{pass } A \\ \underline{000 + 1111} \leftarrow AE \rightarrow b_i = 1 \Rightarrow B = -1 \\ 1001 = 9 = 10 - 1 \checkmark \end{array}$$

(c) K-map for LE:

	ab	00	01	11	10
$\bar{s}_1 s_0$	--A	0	0	1	1
$s_1 s_0$	$A \oplus B$	0	1	0	1
	$A + B$	0	0	1	1
	$A - B$	0	0	1	1

$$\begin{aligned} LE &= \bar{s}_1 s_0 \bar{a} b + s_1 a + \bar{s}_0 a + a \bar{b} \quad \leftarrow \text{answer} \\ &= \bar{s}_1 s_0 \bar{a} b + a(s_1 + \bar{s}_0 + \bar{b}) \\ &= \bar{s}_1 s_0 \bar{a} b + a \bar{s}_1 s_0 b \quad \leftarrow \text{(factor } \bar{a} \text{ from term 1 to reveal XOR)} \\ &= a \oplus (\bar{s}_1 s_0 b) \end{aligned}$$

Challenge question: Why is this answer expected given the LE column (hint: 3 rows output just A)?


2. (4 points) In binary, multiply $A=1010$ by $B=1011$, showing all 4 properly shifted intermediate products. Calculate the overall sum, showing the correct number of output bits needed to handle the largest possible product. In decimal, confirm whether your results agree with $10 \times 11 = 110$

$$\begin{array}{r} 1010 \\ \times 1011 \\ \hline 1010 \\ 1010 \\ 0000 \\ 1010 \\ \hline 01101110 \end{array}$$

64 32 8 4 2
└───┘ └───┘
96 14
└────────┘
110 ✓

CE-1901-12 - Dr. Durant - Quiz 8
Fall 2016, Week 9 Quiz

1. (6 points) ALUs

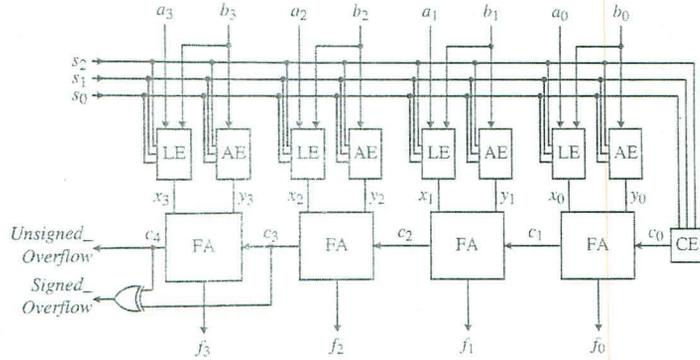

a. (2 points) **Complete** the following table for a 4-operation ALU (an 8-operation ALU is shown for reference):

S	Operation	Expression	LE (FA:a)	AE (FA:b)	CE (FA0:c _i)
0	NOR	$(A \text{ OR } B)'$	$\overline{A+B}$	0	0
1	XOR	$A \oplus B$	$A \oplus B$	0	0
2	Subtract	$A - B$	A	B'	1
3	NAND	$(AB)'$	\overline{AB}	0	0

b. (2 points) **Explain** why the given extender values for subtract are correct. **Provide** an example where the input $A = 1010$ and $B = 0111$.

c. (2 points) **Design** the LE using a K-map.

(b) $A - B \Rightarrow +A - B$
 $\xrightarrow{2's \text{ comp.}} +A + \overline{B}$
 $1 \leftarrow CE \Rightarrow c_0 = 1$
 $1010 \leftarrow A$
 $+ 1000 \leftarrow \overline{B}$
 $\hline 0011 \leftarrow 3 = 10 - 7 \checkmark$

(c) K-map for LE:

	ab	00	01	11	10
s ₁ s ₀	00	1	0	0	0
01	0	1	0	1	
11	1	1	0	1	
10	0	0	1	1	

$LE = \overline{s_1} \overline{s_0} \overline{ab}$
 $+ s_1 s_0 \overline{a}$
 $+ s_0 \overline{a} b$
 $+ s_0 a \overline{b}$
 $+ s_1 s_0 a$

add this one; there are 2 correct options

2. (4 points) In binary, multiply $A=0110$ by $B=1001$, showing all 4 properly shifted intermediate products. Calculate the overall sum, showing the correct number of output bits needed to handle the largest possible product. In decimal, confirm whether your results agree with $6 \times 9 = 45$.

~~45~~
54

$$\begin{array}{r} 0110 \\ \times 1001 \\ \hline 0110 \\ 0000 \\ 0000 \\ 0110 \\ \hline 00110110 \end{array}$$

32 16 4 2
└───┘ └──┘
48 6
└──────────┘ = 54 = 6 × 9 ✓