
Open: book, notes, assembler/disassembler, previous quizzes, Internet. But, do not discuss the quiz with anyone except the professor until after everybody's work is submitted and the due date has passed. Please submit in Teams Assignments.

Given the instruction add r8, r9, #0x4C, that r8 contains 0xFACE and r9 contains 0xBEEF, label the single-cycle processor below taken from Figure 7.17 of your book with

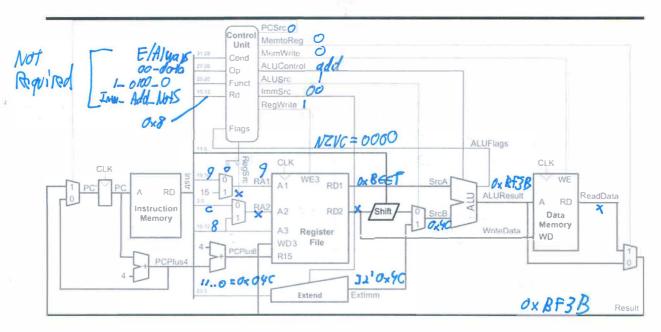- All control signals (X if don't care; for non-MUXes use meaningful name, e.g. add, eor, etc. for ALUControl; don't forget RegSrc; active-high)
- All relevant datapath values (e.g., if ALUFlags aren't used, you can leave them unlabeled) except PC-related values and control unit Instr inputs




add r8, r9, #0x4C Rd Ro Imm8

ALU: Ox BEEF Ox 9C 0000\_BF3R

Given the instruction ldr r13, [r5,#-0x300], that r5 contains 0x1164, and that r13 contains 0x2C04, label the single-cycle processor below taken from Figure 7.17 of your book with

- All control signals (X if don't care; for non-MUXes use meaningful name, e.g. add, eor, etc. for ALUControl; don't forget RegSrc; active-high)
- All relevant datapath values (e.g., if ALUFlags aren't used, you can leave them unlabeled) except PC-related values and control unit Instr inputs
- If you need an unknown register or memory value, indicate it with angle brackets, e.g., <r10> for the unknown value of r10, or <m[0x1C00]> for the unknown, 32-bit word stored in memory starting at 0x1C00.

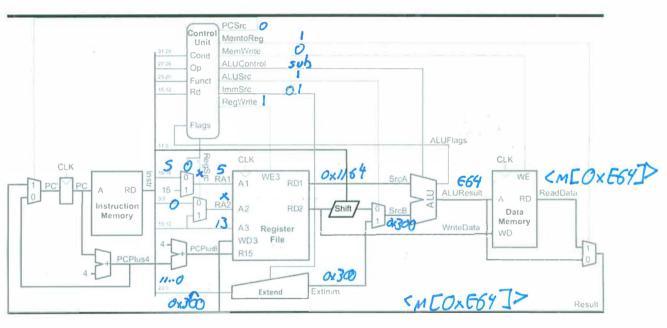

ALC: 0×1/64 -0x 300 000-0E64