

1. Design a single inverter CMOS output stage, such that t_d (delay time) is $20 \text{ ns} \pm 10\%$ for $C_L = 50 \text{ pF}$. Delay time is defined as the time between the input reaching $V_{DD}/2$ and the output reaching $V_{DD}/2$. For this step, the input is voltage into the output stage and the output is the load capacitor.
2. To your circuit from step 1, add your previously designed IBUF ($V_{inv} = 1.4 \text{ V} \pm 10\%$) and your previously designed core logic inverter. Find the overall delay time for this circuit.
3. Now, between the core and the final output stage, add 1 or more inverting stages as needed in a super buffer configuration. Find the overall delay time for this circuit and compare to part 2. (It should go down.)
4. Design a BiCMOS inverter for driving a capacitive load of 50 pF . The maximum frequency of operation must exceed 25 MHz . Simulate using PSPICE.
5. Tristate the output of part 4 by effectively grounding the base current of the BJTs per a tristate control signal. The NMOS transistor that grounds the base of the sourcing BJT must be sized large enough so that it pulls the base below 0.7 V (it forms a voltage divider with the PMOS of the inverter when the inverter output is a logic 1).

Note: For each circuit, you may need to add an extra core inverter to ensure the overall circuit is an inverter.

Use the T15D model from MOSIS ($\lambda = 0.30 \text{ } \mu\text{m}$) for the NMOS and PMOS transistors.

Use the following model, available at <http://iesg.eecs.berkeley.edu/ee105/Overview.fm5.html> and on the course website, for the bipolar transistor:

*Bipolar Transistors

*3505S (similar to 3500, 3501) vertical NPN

```
.model 3505S NPN IS=5.65E-17 RB=465 RE=0.495 RC=41.5 CJE=0.555p
+CJC=0.155p CJS=0.205p BF=94.5 VAF=50.0 BR=0.720 VAR=4.40 VJE=0.960
+MJE=0.330 VJC=0.730 MJC=0.520 VJS=0.450 MJS=0.330 TF=39.0p TR=1.00n
```

PSPICE Note: PSPICE does not like model names starting with a numeric character. The first character in a model name must be an alphabetic character. Add the letter B for Bipolar in front of the model name.

Report Requirements:

1. Show design calculations.
2. Submit all schematics.
3. Submit DC transfer curves for both the overall super buffer circuit and the BiCMOS circuit.
4. Display the I_{DS} and V_{DS} curves vs. time for both PMOS and NMOS output transistors and label the max current. Display a similar graph for the BiCMOS circuit.
5. Based on the calculated delay time for the 2 main circuits, determine the maximum frequency of operation for the specified load.
6. Discuss results

Due: Friday of Week 8 (for both sections)